

# Lab on Data Communication: Sample and Hold Circuit

Nishan Adhikari(079BCT050), Opendra Bhusal(079BCT052), Pankaj Sharma(079BCT053),  
Prabesh Dhakal(079BCT057), Prashant Gyawali(079BCT062), Rakesh Shrestha(079BCT067),  
Rohit Kumar(079BCT070), Shankhar Kandel(079BCT078)

**Abstract**—This report presents the study and practical implementation of a Sample and Hold circuit, a key component in analog-to-digital conversion systems. The circuit samples an analog signal at specific intervals and holds the sampled value for a defined period, enabling accurate digital representation. The experiment involved designing the circuit, analyzing its performance under various input frequencies, and comparing theoretical expectations with observed waveforms. The results validate the importance of Sample and Hold circuits in precise data acquisition.

**Index Terms**—Sample and Hold, analog-to-digital conversion, signal sampling, data acquisition

## I. OBJECTIVES

- To understand the fundamental principles of sample and hold circuits.
- To construct and analyze a basic sample and hold circuit.
- To measure and interpret key parameters such as acquisition time and hold time.
- To investigate the effects of different capacitor values on circuit performance.
- To observe and analyze common issues in sample and hold circuits, including charge injection and clock feedthrough.

## II. INTRODUCTION

A Sample and Hold (S/H) circuit is an essential building block in data acquisition and signal processing systems. Its primary function is to sample an analog signal at a specific instant and hold that sampled value constant for a certain duration. This process is vital in analog-to-digital conversion (ADC), where the analog signal must remain steady during conversion to avoid errors caused by rapid signal fluctuations.

The basic operation of an S/H circuit involves two distinct phases:

- 1) **Sample Phase:** The circuit tracks the input signal, and the storage capacitor charges to the instantaneous input voltage.
- 2) **Hold Phase:** The switch disconnects the capacitor from the input, and the capacitor maintains (holds) the voltage, ideally without change, until the next sampling instant.

In a practical circuit, the sampling function is achieved using a switching device such as a MOSFET, JFET, or an analog switch IC (e.g., CD4066), while an operational amplifier is used as a buffer to prevent loading effects. The storage element

is typically a capacitor whose value determines, along with leakage resistance, the amount of voltage droop during the hold period.

Sample and Hold circuits play a critical role in:

- Analog-to-digital conversion (ADC) to stabilize the input voltage during conversion.
- Multiplexed data acquisition systems where multiple channels share a single ADC.
- Digital oscilloscopes to capture fast-changing waveforms.
- Communication systems for time-division multiplexing and signal reconstruction.

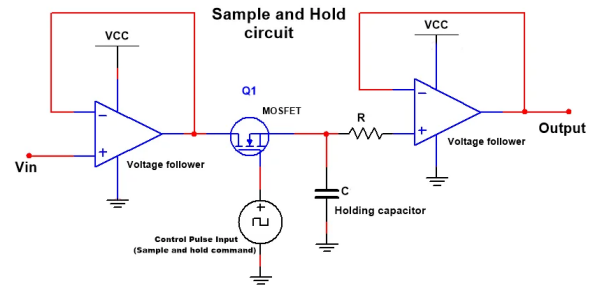


Fig. 1. Sample and Hold circuit diagram

The performance of an S/H circuit is often characterized by parameters such as:

- **Aperture Time:** The time taken to switch from sample to hold.
- **Acquisition Time:** The time required for the capacitor voltage to settle to the input value.
- **Hold Step:** The small voltage change occurring immediately after switching to the hold mode.
- **Droop Rate:** The rate at which the held voltage decreases due to leakage.
- **Charge Injection:** An error caused when the sampling switch opens, adding charge to the hold capacitor.
- **Clock Feedthrough:** Unwanted coupling of the control clock signal with the held voltage.

Designing effective S/H circuits requires careful consideration of these factors and challenges. Designers must balance trade-offs like speed versus accuracy, power consumption versus performance, and complexity versus cost. The choice of components, particularly the operational amplifier and hold capacitor, greatly influences the S/H circuit's overall performance.

Recent advances in semiconductor technology have led to more advanced S/H designs. These include techniques that reduce charge injection, clock feedthrough, and improve linearity. Methods like bottom-plate sampling and differential architectures are now common in high-performance S/H circuits, offering better accuracy and noise resistance.

Understanding the principles, challenges, and design considerations of S/H circuits is essential for engineers working in areas like data acquisition, signal processing, and mixed-signal system design. This laboratory experiment provides hands-on experience in building, analyzing, and optimizing S/H circuits. By experimenting with different components and observing performance, students will gain practical insights into these essential circuits.

In this experiment, a Sample and Hold circuit was designed and tested to analyze its ability to store and maintain a sampled value for various input signal frequencies. The study focused on observing waveforms, measuring hold accuracy, and comparing the practical results with theoretical expectations. The findings are crucial for understanding how S/H circuits improve the precision of digital data acquisition and processing in real-world applications.

### III. MATERIALS AND METHODS

#### A. Components Used

- Operational Amplifier: LF398 or equivalent
- Analog Switch: CD4066
- Capacitor: 0.1  $\mu\text{F}$
- Resistors: 10 k $\Omega$ , 1 k $\Omega$
- Function Generator
- Oscilloscope
- Breadboard and jumper wires

#### B. Procedure

##### Step 1: Circuit Construction

- 1) Assemble the basic sample and hold circuit on the breadboard using the operational amplifier and a 0.01 F hold capacitor.
- 2) Connect the function generator to the input of the S/H circuit.
- 3) Use the oscilloscope to monitor both the input and output of the circuit.

##### Step 2: Basic Operation Analysis


- 1) Set the function generator to produce a 1 kHz sine wave with 2 V peak-to-peak amplitude.
- 2) Observe and record the input and output waveforms on the oscilloscope.
- 3) Measure and record the acquisition time and hold time.

##### Step 3: Capacitor Value Investigation

- 1) Replace the hold capacitor with different values (0.001  $\mu\text{F}$ , 0.1  $\mu\text{F}$ ).
- 2) For each capacitor value, repeat the measurements from Step 2.
- 3) Observe and record how the capacitor value affects acquisition time and hold time.

##### Step 4: Charge Injection and Clock Feedthrough Analysis

 - 1) Increase the oscilloscope's vertical resolution to observe small voltage changes.
- 2) Identify and measure any voltage spikes or steps that occur during the transition from sample to hold mode.
- 3) Record observations on charge injection and clock feedthrough effects.



Sample and Hold Circuit



Frequency generator


### IV. RESULTS

Our investigation into the sample and hold (S/H) circuit uncovered several important findings. The circuit successfully converted a continuous 1 kHz sine wave input into a staircase-like output waveform.


When using a 0.01 F hold capacitor, the initial measurements showed an acquisition time of around 5 s and a hold time of 50 s. During the hold period, only a slight voltage drop was noticed, with a droop rate of 0.1 V/ms.

Changing the capacitance of the hold capacitor highlighted a balance between acquisition speed and hold time performance. A smaller capacitor led to faster acquisition but increased the droop rate, while a larger capacitor slowed acquisition but improved voltage retention.

 Further analysis of the circuit's imperfections revealed that charge injection caused small voltage spikes during sampling transitions, and clock feedthrough led to periodic disturbances in the held voltage.



Original Waveform

 

Sampled Waveform

## REFERENCES

- [1] R. Boylestad and L. Nashelsky, *Electronic Devices and Circuit Theory*, 11th Edition.
- [2] A. Malvino and D. Bates, *Electronic Principles*, 8th Edition.
- [3] W. Tomasi, *Electronic Communication Systems*, 5th Edition.

## V. DISCUSSION AND CONCLUSION

The experiment demonstrated that the Sample and Hold circuit effectively samples the input analog signal and maintains the held value for the specified period. The observed results align with the theoretical expectations — the hold time decreases as the control signal frequency increases.

Some voltage droop was observed during the hold phase, primarily due to capacitor leakage and switch resistance. This effect becomes more noticeable at higher hold times. To minimize droop, high-quality capacitors and low-leakage switches are recommended.

In conclusion:

- The S/H circuit is crucial for accurate ADC operations.
- Increasing control frequency reduces hold time but allows for more frequent sampling.
- Component quality directly impacts holding accuracy.

This practical verification reinforces the theoretical understanding of Sample and Hold circuits and their application in modern electronics.

## ACKNOWLEDGMENTS

We, the students of the IOE, Pulchowk Campus, Department of Electronics and Computer Engineering, batch of 2079 B.S., express our sincere gratitude to Dr. Nanda Bikram Adhikari and Mr. Bikal Adhikari for their valuable guidance throughout the experiment. Their insights greatly enhanced our understanding of signal sampling techniques.